

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
FIFTH SEMESTER B.TECH DEGREE EXAMINATION, APRIL 2018

Course Code: AE303

**Course Name: ELECTRICAL MEASUREMENTS AND MEASURING INSTRUMENTS
(AE)**

Max. Marks: 100

Duration: 3 Hours

PART A

Answer any two full questions, each carries 15 marks

Marks

- 1 a) The function switch for an analog instrument is set to 50 mA and the instrument accuracy is specified as $\pm 1\%$. If the instrument indicates 38 mA, find relative error in measurement. (4)
- b) Define the term probable error as related to measurements. For the case of a large number of measurements in which only random errors are present, determine the probable measurement error if the standard deviation is 0.0014. (4)
- c) An 820 ohm resistance known to be accurate to $\pm 10\%$ carries a 10 mA current. The current was measured on the 25 mA range of an analog ammeter that has an accuracy of $\pm 2\%$ of full scale. Calculate the power dissipated in the resistor and also determine the maximum percentage error. (7)
- 2 a) Sketch the basic construction of a typical permanent magnet moving coil instrument. Label each part of the instrument and explain its operation. (8)
- b) Draw circuit diagram and show how a permanent magnet moving coil instrument can be used as a dc ammeter with a measured current greater than the meter current. (4)
- c) A moving coil milliammeter having a resistance of 10 ohms gives full scale deflection when a current of 5 mA is passed through it. Explain how this instrument can be used for measurement of current up to 1 A. (3)
- 3 a) Write the construction, principle and working of a thermocouple instrument for electrical measurements. Write advantages and disadvantages of using thermocouple instruments for electrical measurements. (8)
- b) Draw the circuit of a rectifier ammeter and explain its working. Write the need for current transformer in this circuit. (7)

PART B

Answer any two full questions, each carries 15 marks

- 4 a) Explain operation of Wheatstone's bridge and derive the balance equation, draw the circuit diagram showing all voltage drops and branch current. Write one application of Wheatstone's bridge. (8)
- b) Draw the Thevenin equivalent circuit of a Wheatstone bridge as seen from the galvanometer. Derive the equation for galvanometer current. Explain what is meant by the sensitivity of a Wheatstone bridge. (7)
- 5 a) Explain working of Kelvin bridge and derive the equation for unknown resistance. (8)

- b) Draw the circuit diagram of Schering bridge and write the balance equation and function of each component. Also explain how it can be used for high voltage measurements. (7)
- 6 a) Explain operation of Maxwell bridge for measuring L in terms of C. Draw the circuit diagram and derive the equation for the inductance being measured. (8)
- b) Explain Anderson bridge with circuit diagram and write how it differs from a Maxwell bridge. (7)

PART C

Answer any two full questions, each carries 20 marks

- 7 a) Draw basic block diagram and explain working of a digital storage oscilloscope for sampling a waveform and storing the information. Show the waveforms that occur at each point. (10)
- b) Explain the working of LCD flat panel display as used in DSO, with suitable diagram to show its construction. (10)
- 8 a) Explain with a block diagram the working of swept super-heterodyne spectrum analyser. (10)
- b) Draw basic circuit diagram of a Q meter and explain its operation. (10)
- 9 a) Draw block diagram for a fundamental suppression distortion meter and explain the system operation. (10)
- b) Show how instrument transformers may be used to extend the range of a wattmeter. Explain the circuit and write the multiplication factor. (10)
